

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Third Semester of B. Tech. Examination (EC)

November 2013

EC202 Network Theory

Date: 23.11.2013, Saturday

Time: 01:30 p.m. To 04:30 p.m.


Maximum Marks: 70

Instructions:

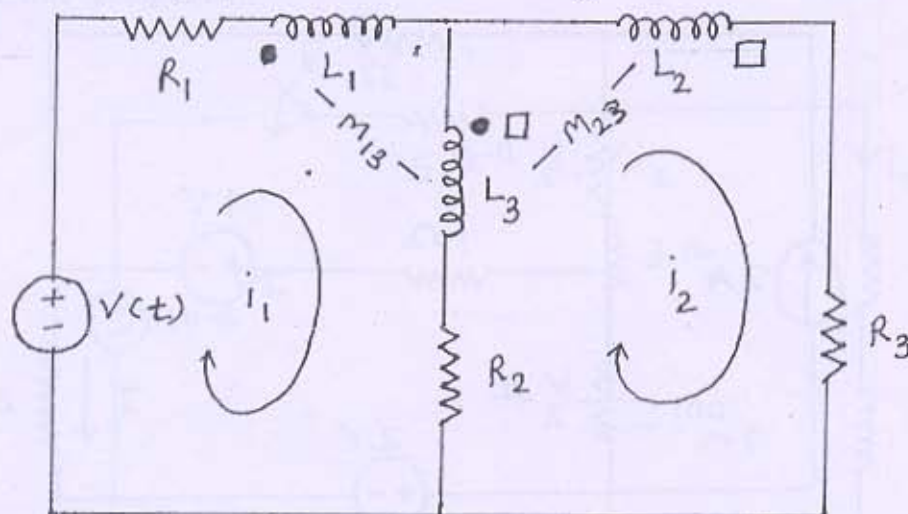
1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION - I


Q - 1 (a) A network with magnetic coupling is shown in following figure, For the network [07]
 $M_{12}=0$. Write loop equations for this network using KVL.



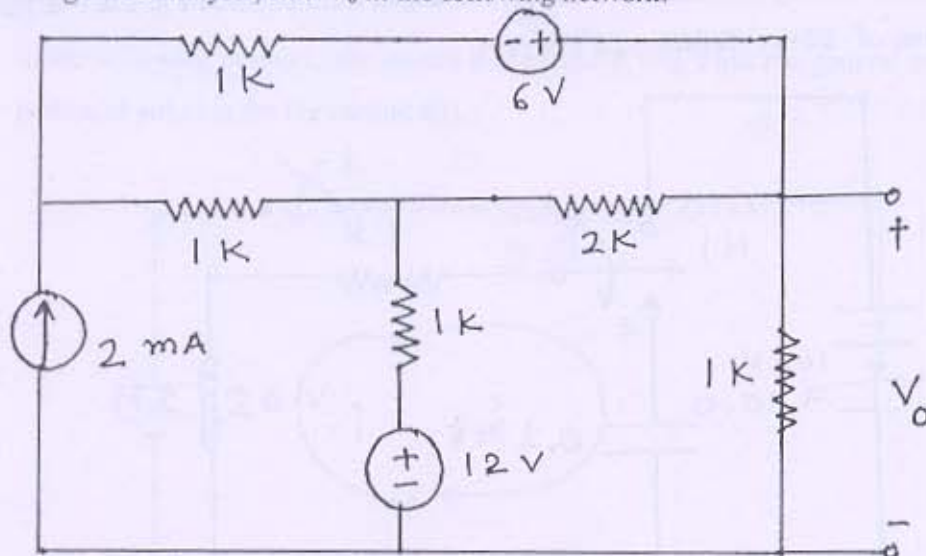Q - 2 (a) Using mesh analysis, find V_0 in the following network. [14]




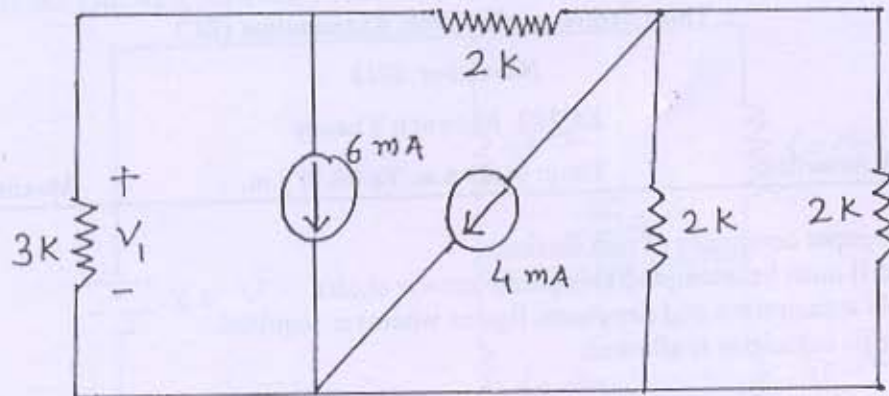(b) Using node analysis, find V_1 in the following network.




OR

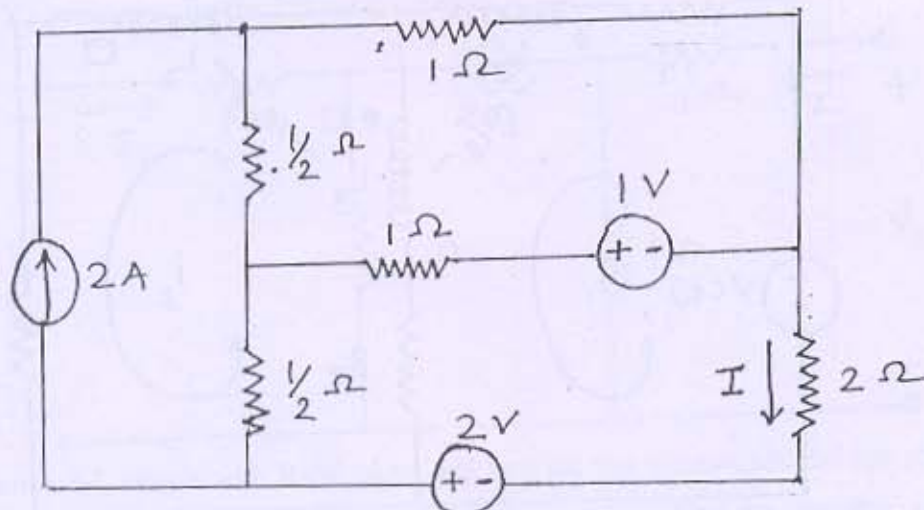
Q-2 (a) In the following network, Determine the branch current I using source transformation method. [14]



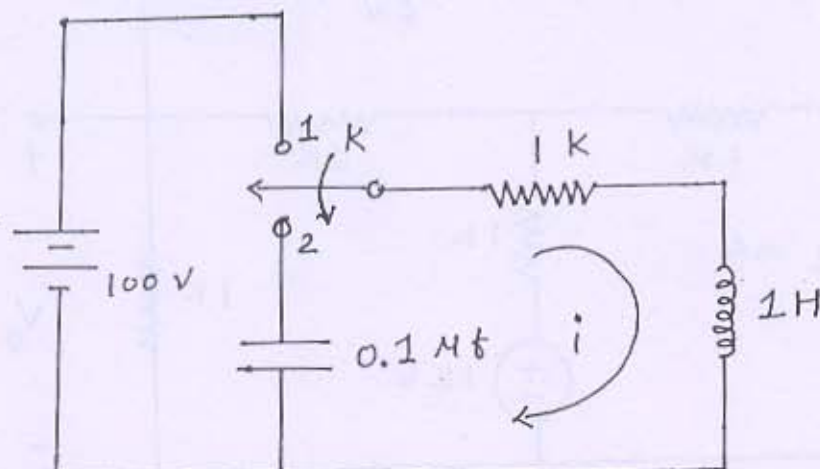
(b) In the following network, the switch k is changed from position 1 to 2 at $t=0$. Find values of $i(0^+)$, $di/dt(0^+)$, $d^2i/dt^2(0^+)$.



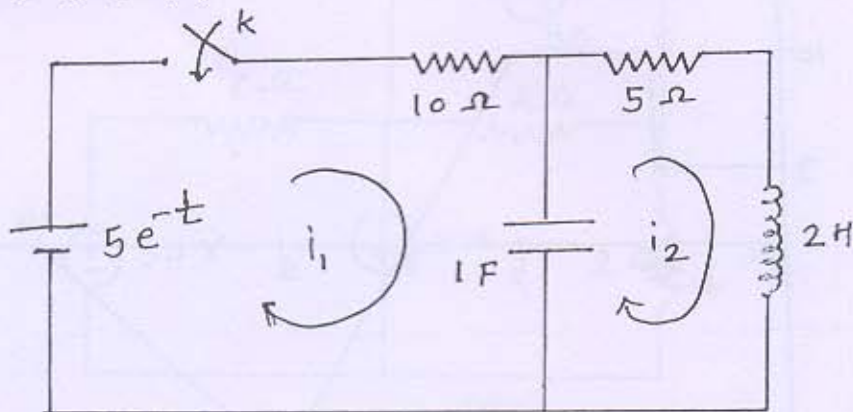Q - 3 (a) In the following network, the switch k is closed at $t=0$. Find values of $i_1(0+)$, $i_2(0+)$, $\frac{di_1}{dt}(0+)$, $\frac{di_2}{dt}(0+)$. [14]




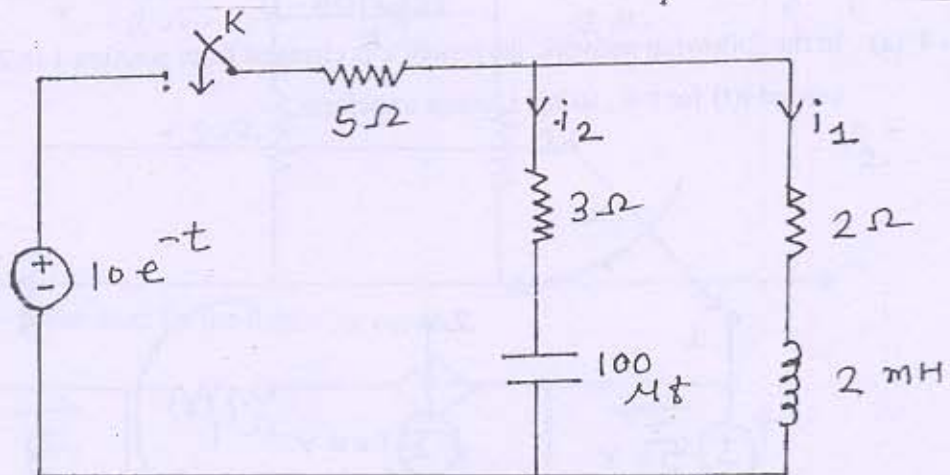(b) In the following network, the switch k is closed at $t=0$. Find values of $i_1(0+)$, $i_2(0+)$, $\frac{di_1}{dt}(0+)$, $\frac{di_2}{dt}(0+)$.




OR

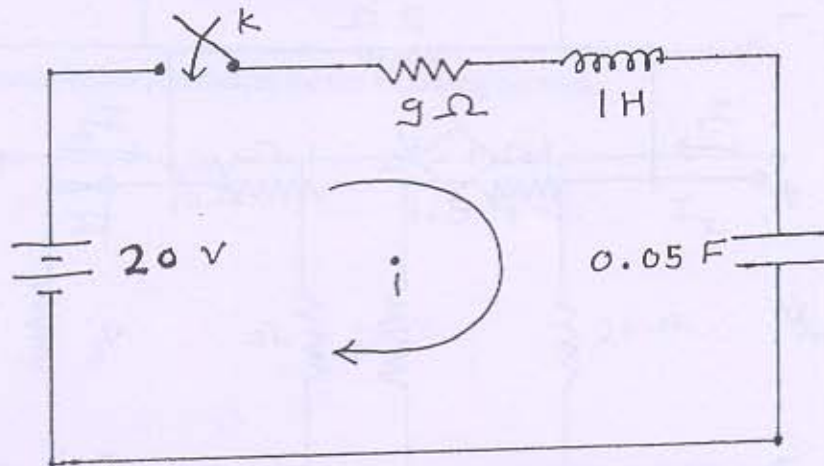Q - 3 (a) In the following network, the switch k is closed at $t=0$. Find the general solution and particular solution for the current $i(t)$. [14]




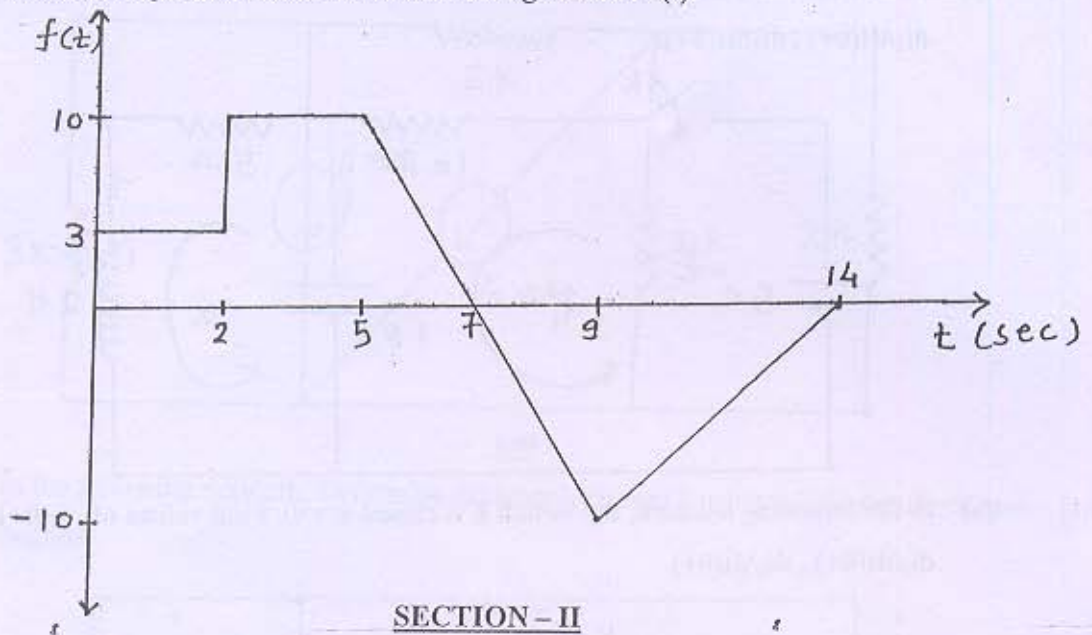(b) Find the Laplace transform of the following function $f(t)$.




SECTION - II

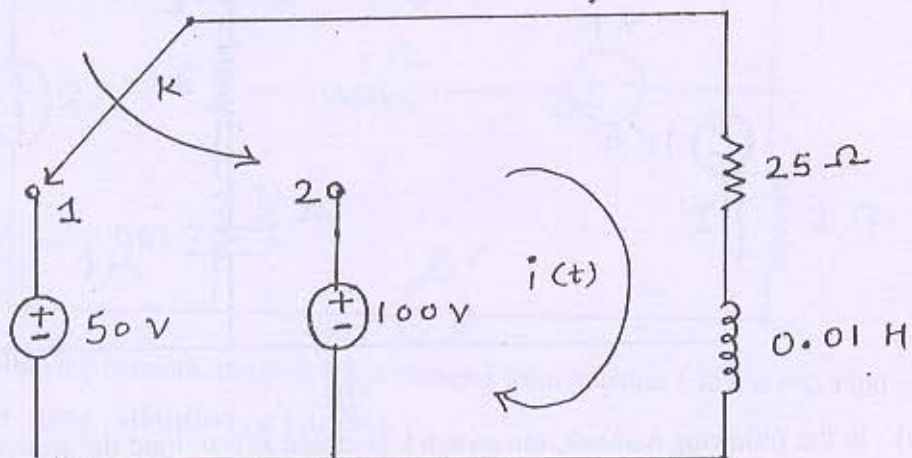
Q - 4 (a) In the following network, the switch k is changed from position 1 to 2 at $t=0$. Find the current $i(t)$ for $t>0$, using Laplace transform. [07]



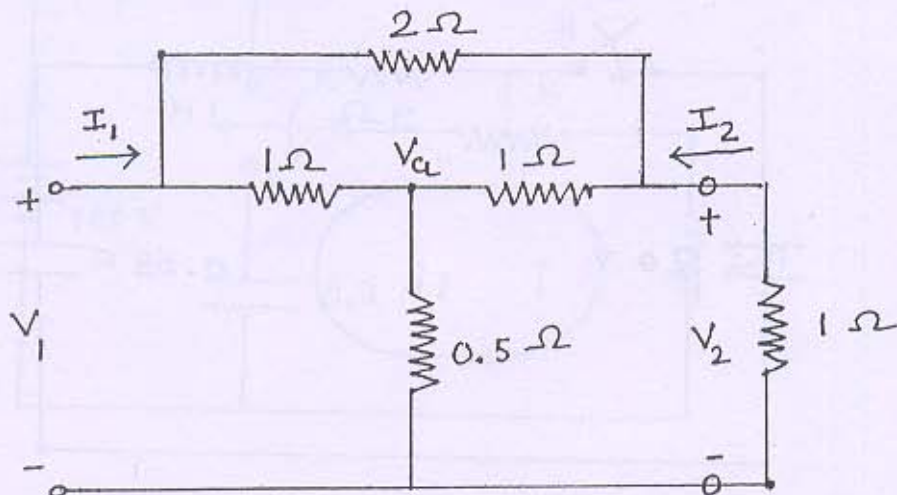Q - 5 (a) In the following two port network, Find the value of G_{12} . [14]



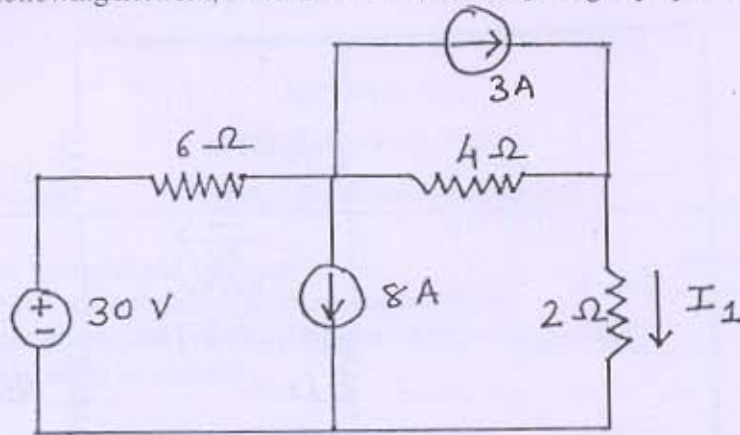
(b) In the following network, Determine the value of I_1 using superposition theorem.




OR

Q - 5 (a) Find Z - parameters for the following network.

[14]

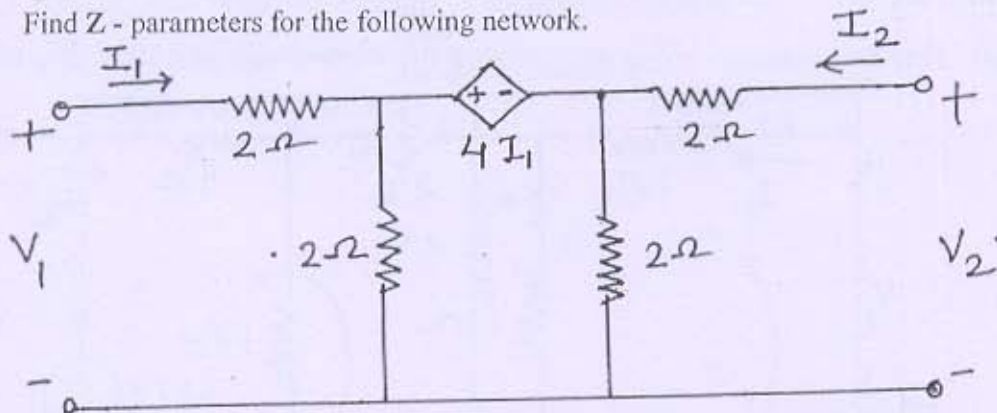


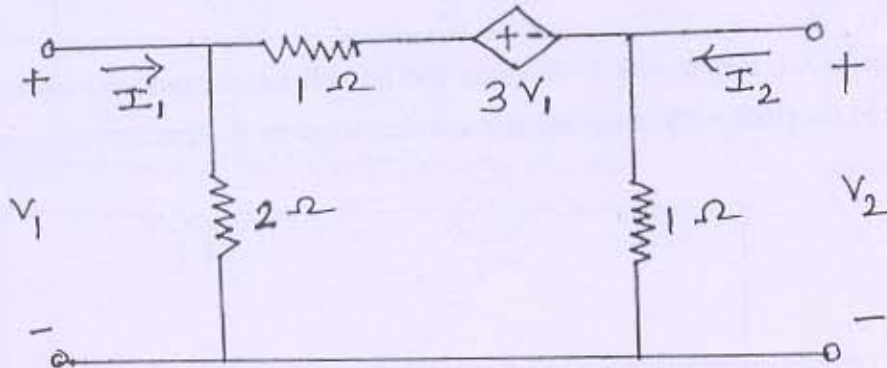(b) Find Y - parameters for the following network.




Q - 6 (a) Find Transmission parameters for the following network.

[14]

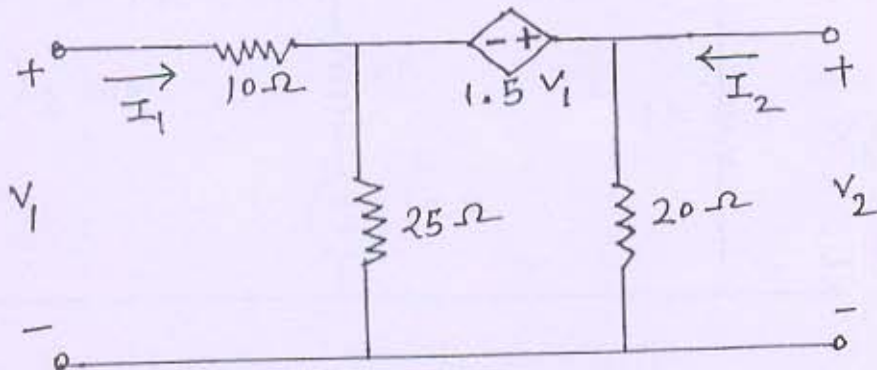

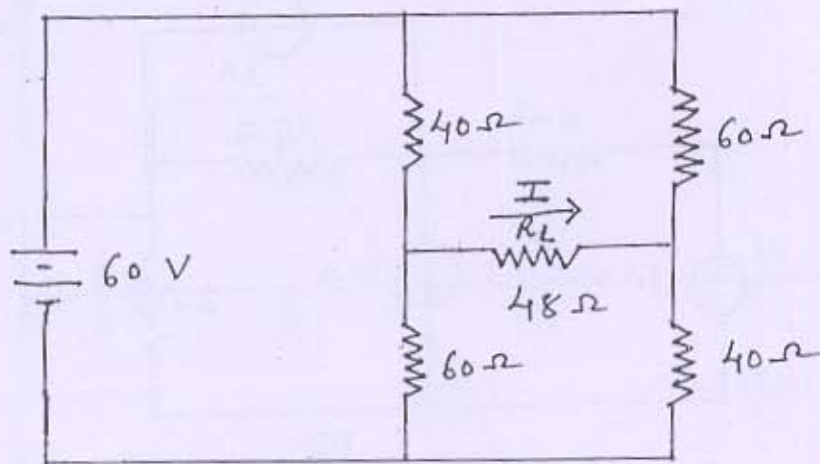
- (b) In the following network, Find the current I using Thevenin 's theorem.



OR

- Q - 6 (a) Find Y - parameters for the following network.

[14]

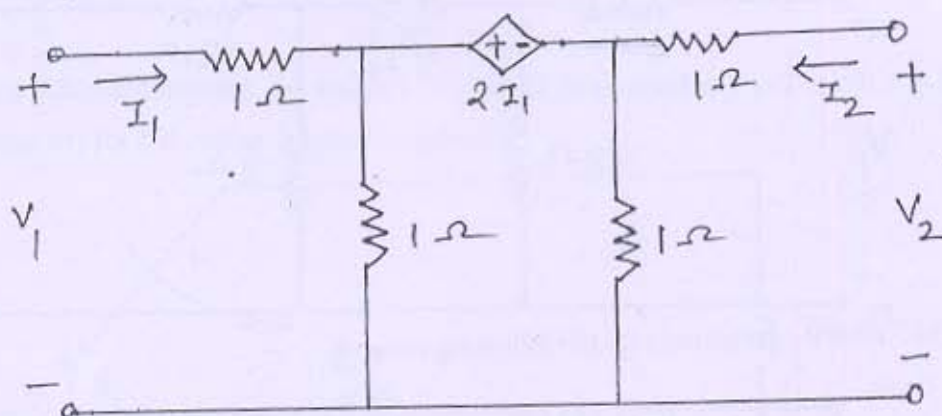

- (b) In series R-L circuit with $R=50$ ohms and $L=0.2$ H has a sinusoidal voltage source $V=150 \sin (500t + \Theta)$ volts applied at a time when $\Theta=0$. Find the complete current transient.