

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Third Semester of B. Tech. Examination (EC)

April/May 2012

EC203 Solid State Electronics

Date: 03.05.2012, Thursday

Time: 01:30 p.m. To 04:30 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections and Use of scientific calculator is allowed.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required

SECTION - I

- Q - 1 (a) Describe following terms briefly [03]
- (i) Thermistor
 - (ii) Sensor
 - (iii) Photoconductor
- (b) What is mobility? Derive equation for current density J and conductivity σ . [04]
- Q - 2 (a) Prove that Fermi level lies in center of forbidden energy band in intrinsic semiconductor. [07]
- (b) Why Silicon is prefer over Germanium in IC fabrication. Also mention advantages of Ge over Si. [03]
- (c) The amplifier of figure 1 utilizes an n-channel FET for which $V_p = -2.0$ V and $I_{DSS} = 1.65$ mA. It is desired to bias the circuit at $I_D = 0.8$ mA, using $V_{DD} = 24$ V. Assume $r_d \gg R_d$. Find V_{GS} , g_m and R_s . [04]

OR

- (c) The Fixed bias configuration of figure 2 had an operating point defined by $V_{GSQ} = -2$ V and $I_{DQ} = 5.625$ mA with $I_{DSS} = 10$ mA and $V_p = -8$ V. For $y_{os} = 40$ μ S find out g_m , r_d , z_i , z_o and A_v . [04]
- Q - 3 (a) Classify amplifiers on the bases of operation method (Q point) and also mention application of amplifier. [07]
- (b) Draw and Explain V-I characteristic of idle p-n junction diode. [03]
- (c) Discuss RC coupled multistage amplifier. [04]

OR

- (c) Discuss Reverse Saturation Current, Rise Time, Tilt and square wave testing. [04]

SECTION - II

- Q - 4 (a) Define following terms [03]
- (i) Cutin voltage in diode
 - (ii) Avalanche multiplication
 - (iii) Photovoltaic potential
- (b) Explain Full wave rectifier using diode [04]
- Q - 5 (a) Find the transistor currents in the figure 3. A silicon transistor with $\beta = 100$ and $I_{CO} = 20$ nA is under consideration. Also Repeat same if 2 k Ω emitter resistance is provided (figure 4). [07]

OR

- Q - 5 (a) Consider the transistor common emitter amplifier and the h parameters are given in table 1. If $R_L = 10K$ and $R_S = 1K$, find the various gains and input and output impedance. [07]
- (b) Explain Early effect/ Base width modulation. [04]
- (c) Explain Thermal Runaway. [03]
- Q - 6 (a) Explain the "h Parameter" analysis of a transistor amplifier. [07]

OR

- (a) Explain the "hybrid - π " model for conductance and resistance. [07]
- (b) Compare CE and CC configuration. [04]
- (c) Explain Ebers-moll model for p-n-p transistor. [03]

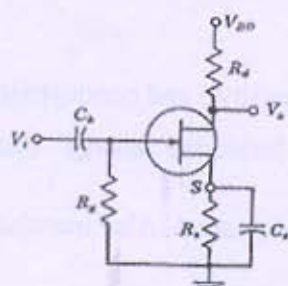


Figure-1

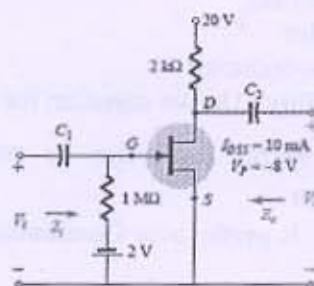


Figure-2

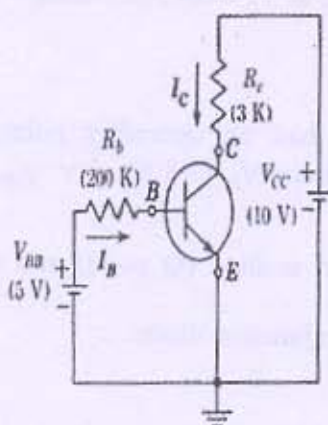


Figure-3

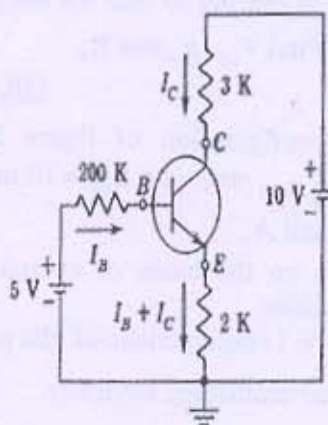


Figure-4

Parameter	CE	CC	CB
h_i	1 k Ω	1 k Ω	20 Ω
h_r	2.5×10^{-4}	≈ 1	3.0×10^{-4}
h_f	50	-50	-0.98
h_o	25 $\mu A/V$	25 $\mu A/V$	0.5 $\mu A/V$
$1/h_o$	40 k Ω	40 k Ω	2 M Ω

Table-1
