

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Third Semester of B. Tech. (EC) Examination

March / April 2018

EC203.01 / EC 203 Solid State Electronics

Date: 02.04.2018, Monday

Time: 1:30 p.m. to 4.30 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Use of scientific calculator is allowed.

SECTION-I

- Q-1 Answer Following Questions [05]**
- (a) Draw Half Wave Rectifier. [02]
- (b) Describe Diode Biasing : Forward and Reverse [03]
- Q-2 Attempt Any Three [15]**
- (a) Draw and explain circuit of fixed bias (base resistor) method for transistor [05]
- (b) Explain the working of NPN transistor with necessary circuit diagram. [05]
- (c) Draw and explain circuit of voltage divider bias method for transistor [05]
- (d) How transistor works as an amplifier? [05]
- Q-3 Attempt Any Three [15]**
- (a) Explain dc load line with Q-point. [05]
- (b) Draw Common Emitter output characteristics. [05]
- (c) Give the difference between FET and BJT [05]
- (d) Explain FET construction, operation and static characteristics [05]

SECTION – II

- Q-4 Attempt Following Questions [05]**
- (a) Difference between JFET and MOSFET [02]
- (b) Explain Pinch off Voltage and Gate to Source Voltage. [03]
- Q-5 Attempt Any Three [15]**
- (a) Draw and explain circuit diagram of direct coupled multi stage amplifier [05]

- (b) Draw and explain circuit diagram of RC coupled multi stage amplifier. [05]
- (c) What is stabilization in transistor? Describe the need of stabilization in detail [05]
- (d) What is stability factor in transistor? Derive mathematical expression of stability factor in transistor. [05]
- (e) Draw input and output characteristics of common base (CB) transistor connection. [05]

Q-6 Attempt Any Three [15]

- (a) Explain the construction and working of metal oxide semiconductor field effect transistor (MOSFET). [05]
- (b) Define: Frequency Response, Decibel Gain and Bandwidth Gain. [05]
- (c) Describe Frequency Distortion. [05]
- (d) Describe Shunt capacitor filter and Choke Input Filter [05]
- (e) Describe Diode in open circuited condition with junction theory and barrier potential concept [05]
