

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY**Third Semester of B. Tech (EC) Examination****November 2014****EC 201.01/EC 201 Digital Electronics & Logic Design****Date: 12.11.2014, Wednesday****Time: 10.00 a.m. To 01.00 p.m.****Maximum Marks: 70****Instructions:**

1. The question paper comprises two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION – I**Q - 1 Answer the question below.****[07]**

- a. Which of the following logics is the fastest?
(a) TTL (c) CMOS
(b) ECL (d) LSI
- b. The decimal equivalent of 10111.0110 is
(a) 22.3 (c) 22.75
(b) 23.75 (d) 23.3
- c. Simplify the Boolean function using K-map. $F(x,y,z)=\sum(0,2,4,5,6)$
- d. Design a half-adder circuit with a decoder and two OR gates.
- e. Perform following operation using 2's complement method $(-46) - (25) = ?$
- f. Mention name of four different methods for control organization.
- g. Define Fan out and Power Dissipation with respect to logic gates.

Q – 2.a Reduce following function using Tabulation Method**[04]**

$$F(w,x,y,z)=\sum(1,4,6,7,8,9,10,11,15)$$

Q – 2.b Answer any two questions.**[10]**

- (i) Implement the given function using Multiplexer.

$$F(a,b,c,d)=\sum(0,1,3,4,8,9,15)$$

- (ii) Write a short note memory unit and explain read and write functions.
- (iii) Explain 4 bit Magnitude Comparator with logic diagram and functions.

Q - 3 Answer any two questions.**[14]**

- a. Simplify following function using K-map and draw logic diagram for reduced function
 $F=A'B'C'+B'CD'+A'BCD'+AB'C'$
- b. Design BCD to decimal decoder with Truth table for 0 to 9 decimal numbers.
- c. Design BCD to Excess-3 code converter with Truth table for 0 to 9 decimal numbers.

SECTION – II

Q - 4 Answer the question below. [07]

- a. State the difference between combinational and sequential circuit.
- b. What is race around condition?
- c. Differentiate between Latch and Flip-flop?
- d. What is master-slave JK flip flop?
- e. Write down the characteristic equation of JK flip flop.
- f. What is the difference between Positive Edge and Positive Trigger clock?
- g. State the difference between ripple counter and synchronous counter?

Q – 5.a Explain the 4 bit Serial input and serial output shift register with proper waveform and diagram. [05]

OR

Q – 5.a Explain static-0 and static-1 Hazard with suitable example. [05]

Q – 5.b Explain block diagram of Processor unit with scratchpad memory. [04]

Q – 5.c Explain Positive edge triggered JK flip flop with truth table and Waveform. [05]

OR

Q – 5.c Explain JK flip flop to SR flip flop conversion. [05]

Q – 6.a What is the Programmable Logic Unit? State the Application of it. [02]

Q – 6.b Design a Mod 5 Synchronous counter using T flip flop. [07]

Q – 6.c Design a counter with following binary sequence: - 0,1,3,7,6,4 and repeat. [05]

OR

Q – 6.c Explain Johnson Counter. [05]
