

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Fourth Semester of B. Tech. Examination (EC)

May 2012

EC 208 Analog Electronic Circuits

Date: 17.05.2012, Thursday

Time: 01:30 p.m. To 04:30 p.m.

Maximum Marks: 70


Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION - I

Q - 1 (a) Calculate the effective resistance seen looking into the primary of a 15:1 transformer [02]
connected to an 8 ohm load.

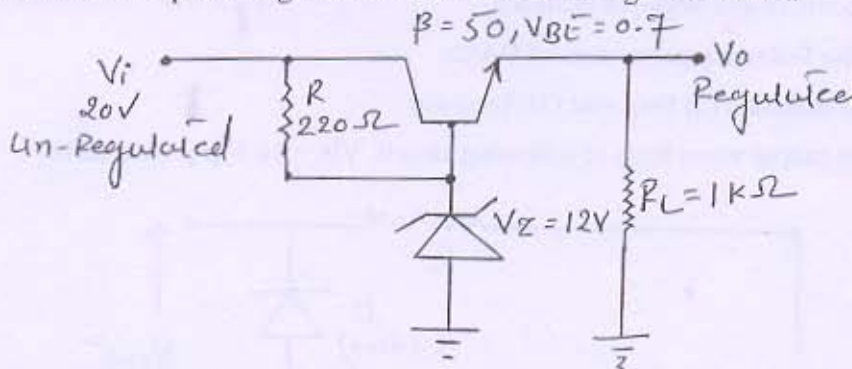(b) Calculate the output voltage and zener current in the regulator circuit. [05]



Q - 2 (a) What is the significant difference between voltage amplifier and power amplifier? [02]

(b) Draw the circuit of an emitter coupled differential amplifier and explain why the [06]
 $CMRR \rightarrow \infty$ for a symmetrical circuit with $R_e \rightarrow \infty$.

(c) Explain the counter type A to D Converter. [06]

OR

Q - 2 (a) Compare the power amplifier classes in terms of their efficiency. [02]

(b) Draw the equivalent circuit from which to calculate common mode gain and [06]
difference gain for the emitter coupled differential amplifier.

(c) Explain the successive approximation type ADC. [06]


Q - 3 (a) What are the four possible topologies of a feedback amplifier? Identify the output [04]
signal X_o and the feedback signal X_f for each topologies

(b) State the three fundamental assumptions which are made in order that the expression [04]

$$A_f = \frac{A}{1 + A\beta} \text{ be satisfied exactly.}$$

(c) Explain weighted resistor type DAC [03]

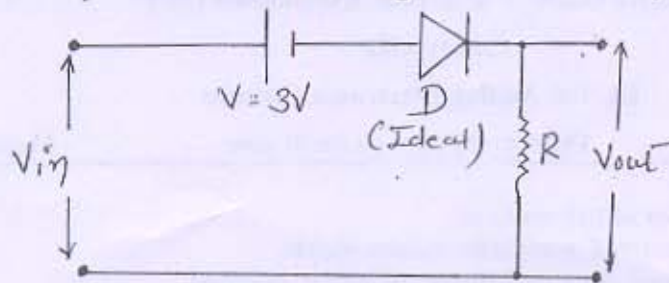(d) Draw the output wave form of following circuit. $V_{in} = 10 \text{ V p-p Sine wave}$. [03]



OR


Q-3 (a) Define desensitivity D. for a large value of D what is A_f ? What is a significance of this result? [04]

(b) Define positive and negative feedback. [04]

(c) Define the following parameters of DACs: [03]

(1) Resolution (2) Step size (3) Accuracy

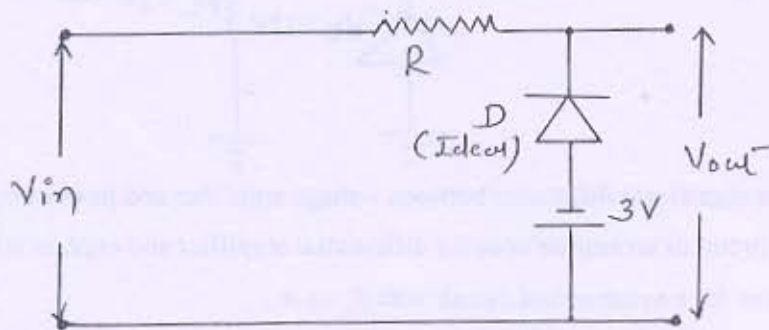
(d) Draw the output wave form of following circuit. $V_{in} = 10 \text{ V p-p Sine wave}$. [03]



SECTION - II

Q-4 (a) What is the condition for the sustained oscillation? [02]

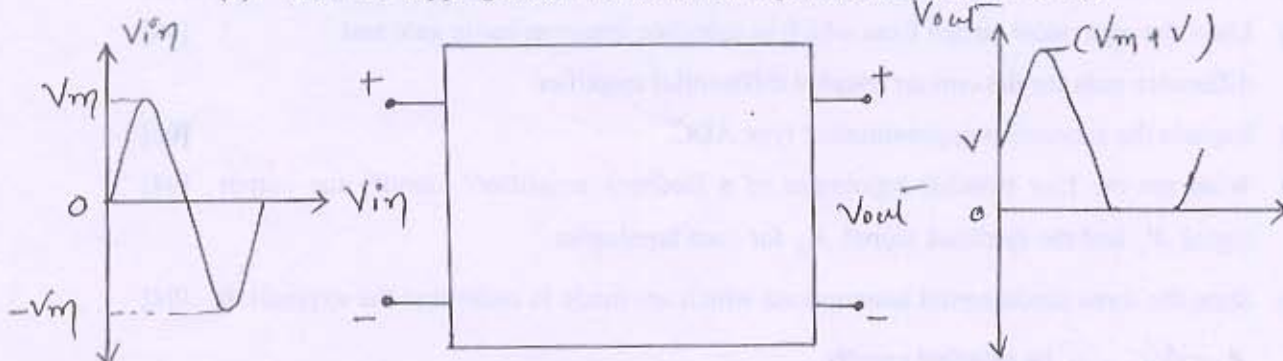(b) Draw the clipping circuit for the below input and output wave forms. [05]




Q-5 (a) Explain the basic principle of RC phase shift oscillator. [02]

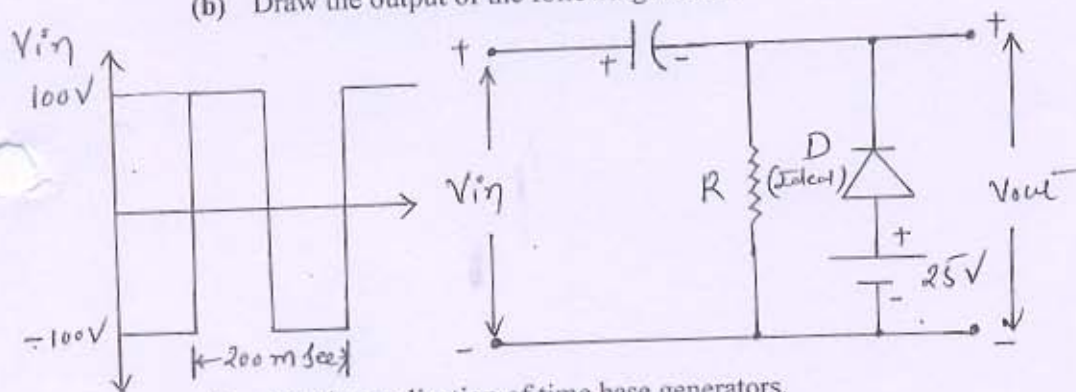- (b) Explain hartly oscillator with necessary circuit diagram. [04]
 (c) Explain the V-I Characteristic of tunnel diode. [04]
 (d) Explain general features of a time base signal. [04]

OR


- Q - 5 (a) Can a negative feedback amplifier work as an oscillator? If yes, how? If no, why? [02]
 (b) Draw and explain the wein bridge oscillator. [04]
 (c) Explain the unijunction transistor. [04]
 (d) Explain the basic principles of miller and bootstrap time base generators. [04]
 Q - 6 (a) Explain Clamping circuit theorem. [03]
 (b) Draw the output of the following circuit. [04]



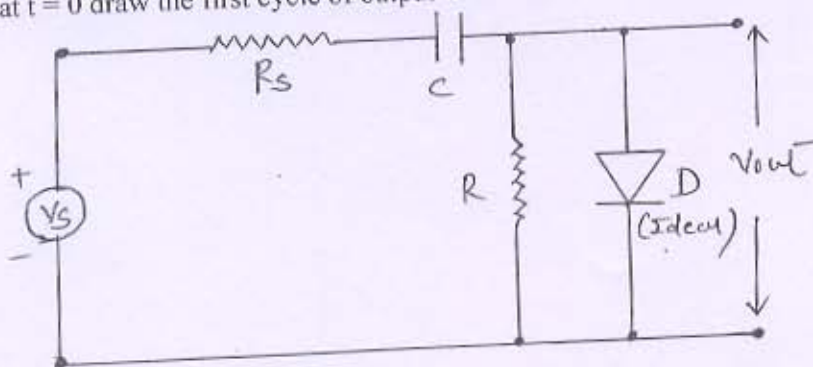- (c) List the application of time base generators. [02]
 (d) Explain a simple current sweep in time base generator. [05]

OR

- Q - 6 (a) In the circuit below $R_s = R_f = 50 \text{ ohm}$, $R = 20 \text{ Kohm}$ and $C = 2 \text{ micro-ferade}$. A symmetrical square wave signal of amplitude 20 volt and frequency 5 KHz is applied at $t = 0$ draw the first cycle of output waveform. [07]



- (b) List the methods of generating a time base wave forms. [02]
 (c) Explain a transistor current time base generator. [05]
