

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Fifth Semester of B. Tech. Examination (EC)

April/May 2013

EC304 Power Electronics

Date: 18.04.2013, Thursday

Time: 10:00 a.m. To 01:00 p.m.

Maximum Marks: 70

Instructions:


1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION – I

Q - 1

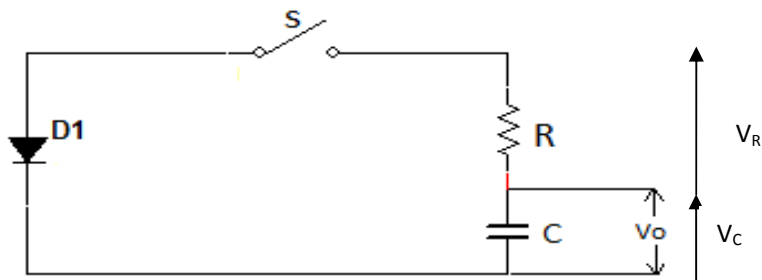- (a) Explain the operation of SCR using two transistor analogy by deriving required equations. [04]
- (b) Justify the statement *“In three phase half wave control rectifier the required minimum firing angle is $\alpha=30^\circ$ ”*. [03]

- Q - 2 (a)** A diode circuit shown in fig. given below with $R=44\Omega$ and $C=0.1\mu F$. The capacitor has an initial voltage, $V_0=220V$. If switch S_1 is closed at $t=0$, determine [04]
- (i) the peak diode current (ii) the energy dissipated in the resistor R



- (b) Enumerate the methods by which SCR can be turned on. [04]
- (c) Explain 1- ϕ bidirectional ac voltage controller with resistive load. Draw necessary diagram and derive output voltage equation. [06]

OR

- Q - 2 (a)** Why heat is generated in within the power devices? Explain electrical analog of heat transfer from a power semiconductor device. [04]
- (b) Explain working principle, application of following thyristor with symbol [04]
- (a) GTO (b) LASCR
- (c) What is cycloconverter ? Discuss its operation principle and sketch the diagram for 1- ϕ to 1- ϕ cycloconverter. [06]
- Q - 3 (a)** What are the types of power diodes? Explain any one in detail. [03]
- (b) Explain how the isolation is accomplished between the thyristor and its gate-pulse-generator circuit. [03]

- (c) Draw and explain 3-Ø half wave control rectifier circuit. Draw its waveform for [08]
 following firing angle
 (a) $\alpha=15^\circ$ (b) $\alpha=45^\circ$

OR

- Q - 3 (a) List the advantages of COOLMOS over conventional MOSFET. [03]
 (b) Discuss the following with respect to BJT [03]
 i) Secondary breakdown ii) Safe operating area
 (c) Explain single phase semi converter for highly inductive load with the help of circuit [08]
 diagram. Draw supply voltage, output voltage waveforms. Write equation for average
 output voltage and RMS value of output voltage.

SECTION – II

- Q - 4(a) List the control strategies for operating the switches employed in DC choppers. [03]
 Explain any one detail.
 (b) Explain the operating modes of DC drives. [04]
 Q - 5 (a) Explain the principle of working of a single phase half bridge inverter with the help of [08]
 the circuit and waveforms for both resistive and inductive loads. Calculate rms output
 voltage at the fundamental frequency and the output power for a dc input voltage of
 48 V and resistive load of 2.4 Ω .
 (b) Classify the chopper. List all types of Chopper and explain any one [06]
 of them.

OR

- Q - 5 (a) Draw and explain the structure of power MOSFET. Also explain principal of [08]
 operation and switching characteristics of power MOSFET.
 (b) Draw and explain the block diagram for microcomputer control of DC drives [06]
 Q - 6 (a) Draw the circuit of boost regulator and explain its working with equivalent circuit and [08]
 waveforms. Obtain equation for ΔI and ΔV_c .
 (b) Explain Single phase Full (Bridge) controlled rectifier with resistive load in detail. [06]

OR

- Q - 6 (a) Describe the operation of 3-phase inverter with 120° conduction. [08]
 (b) What is the principle of operation of step-down converter? Show complete analysis [06]
 of step-down converter with RL load with all necessary diagrams.
