

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Fifth Semester of B. Tech. Examination (EC)

April/May 2012

EC304 Power Electronics

Date: 03.05.2012, Thursday

Time: 10:00 a.m. To 01:00 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION – I

Q - 1 (a) Define (i) Forward recovery time (ii) Reverse recovery time [03]
(iii) Softness factor in power diode.

(b) Draw and explain the SCR in detail also explain SCR V-I characteristics with required terms. [04]

Q - 2 (a) Enumerate the methods by which thyristor is turned on. Explain any two. [04]

(b) Draw a snubber circuit for SCR. How does it provides dv/dt protection? [04]

(c) Explain the working of single phase unidirectional controller. [06]

OR

Q - 2 (a) An SCR with latching current 50 mA is connected in series with resistance of 20Ω and inductance of 0.5H. The duration of the firing pulse is 50μSec. Will the thyristor get fired. [04]

(b) Discuss one quadrant chopper fed dc drive for separately excited dc motor. [04]

(c) Explain the operation of 1-Φ dual converter with waveforms. [06]

Q - 3 (a) Explain the basic parallel inverter with waveforms. [06]

(b) Draw the circuit and output waveforms for 3-Φ Full converter with highly inductive load for firing angle (α) of $\pi/3$. Derive the equations for output DC and RMS voltages for $\alpha \leq \pi/3$. [08]

OR

Q - 3 (a) The forward voltage drop of power diode is $V_D = 1.2$ V at $I_D = 300$ mA. Assuming that $n=2$ and $V_T = 25.8$ mV, Find the saturation current I_s . [03]

(b) Why it is necessary to connect thyristors in parallel? Explain the problems associated with it. How it can be overcome? [03]

(c) Explain the operation of three phase to single phase cycloconverter. [08]

SECTION – II

Q - 4(a) Justify that for high frequency operation MOSFET is used instead of BJT as [03]
switching device.

(b) List two major drawbacks of square wave inverters. How it can be overcome? [04]

Q - 5 (a) Draw the circuit of buck-boost regulator and explain its working with equivalent [08]
circuit and waveforms. Obtain equation for ΔI and ΔV_c .

(b) Explain the operating modes of DC motor. [06]

OR

Q - 5 (a) Explain the operation of 3-phase bridge inverter operating in 120° mode. Draw [08]
appropriate waveforms.

(b) Draw and explain Half wave controlled rectifier with resistive load. Draw the [06]
waveforms. Derive the equations for average load voltage and RMS load voltage.

Q - 6 (a) In a step up chopper applied voltage is 200V and output voltage is 600V. If the [08]
conducting time of thyristor is $200\mu\text{Sec}$, Compute

i) chopper frequency

ii) Find output voltage when the pulse width is half for constant frequency of
operation.

Derive the necessary equations.

(b) Explain the construction and characteristics of IGBT. [06]

OR

Q - 6 (a) Explain the operation of 1-phase bridge inverter with suitable waveforms. Derive [08]
necessary equations.

(b) Write note on Chopper classification. [06]
