

**CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY****Sixth Semester of B. Tech (EE) Examination****October 2017****EE307 Electrical Power System III****Date: 04/10/2017, Wednesday****Time: 01.30 p.m. to 04.30 p.m.****Maximum Marks: 70****Instructions:**

1. The question paper comprises two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

**SECTION – I**

**Q – 1. A** Why single phase representation of balanced three phase network is required for three phase calculation? **[03]**

**B** Explain the function of **[04]**

- (i) Arc runners
- (ii) Arc splitters
- (iii) Magnetic blow out coil.
- (iv) Arcing Contacts

**Q – 2** **Attempt any TWO**

**A** Derive the expression for rate of rise of restriking voltage (RRRV). Find out the time for peak restriking voltage and peak of restriking voltage with necessary circuit and assumptions. **[07]**

**B** With neat and clean diagrams explain the phenomena of current chopping. **[07]**

**C** Write technical note on ionization and deionization of gases. **[07]**

**Q - 3** **Answer any TWO**

**A** With neat diagram explain the construction and working of Air Break Circuit Breaker. **[07]**

**B** With neat diagram explain the construction and working of Vacuum Circuit Breaker. **[07]**

**C** Write technical note on rating of circuit breaker. **[07]**

**SECTION – II**

**Q - 4** State the following statements are TRUE or FALSE. **[07]**

- I. Either referred from HV side or LV side, pu impedance of the transformer remains same.
- II. Neutral impedance has significance effects on Line to Line fault currents.
- III. In a star connected system, without neutral grounding, zero-sequence currents are zero.
- IV. The short circuit current for an unloaded synchronous machine is inversely proportional to its percentage reactance.
- V. For LLG fault, one set of the possible values of sequence components is:  
 $I_{a1}=j1.54$  pu,  $I_{a2}=j1.54$  pu and  $I_{a0}=j1.54$  pu.

- VI. A symmetrically designed generator generates voltage of positive sequence only.  
 VII. The power invariance theorem says that, in all sequence network power remains same.

**Q – 5 Attempt Any Two**

- A** A power station has two alternators of rating 2500 kVA & 5000 kVA and the reactance are 6% and 8% respectively. The circuit breakers are rated 150 MVA. The system is to be extended by taking supply from a grid via transformer of 5000 kVA rating having a reactance of 7.5%. If the same Circuit Breakers are to be used, find the necessary reactance to be placed between the bus-bar and the transformer to protect the switch gear. The voltage of the system at the bus-bar is 3.3 kV. **(Take base KVA= 5000 KVA)** [07]
- B** In a 3-phase 4-wire system, the currents in a, b and c lines under abnormal conditions of loading are as under. [07]  
 $I_a = 100\angle 30^\circ \text{ A}$ ,  $I_b = 50\angle 300^\circ \text{ A}$ ,  $I_c = 30\angle 180^\circ \text{ A}$   
 Calculate sequence currents in a line and neutral current.
- C** Derive the sequences impedances of transmission line. [07]

**Q – 6 Attempt Any Two**

- A** A part of power system is shown in figure 1. The ratings of equipments are indicated in figure. Calculate the fault current at shown location for double line to ground fault. **(Take base as per generator 1 Rating.)** [07]

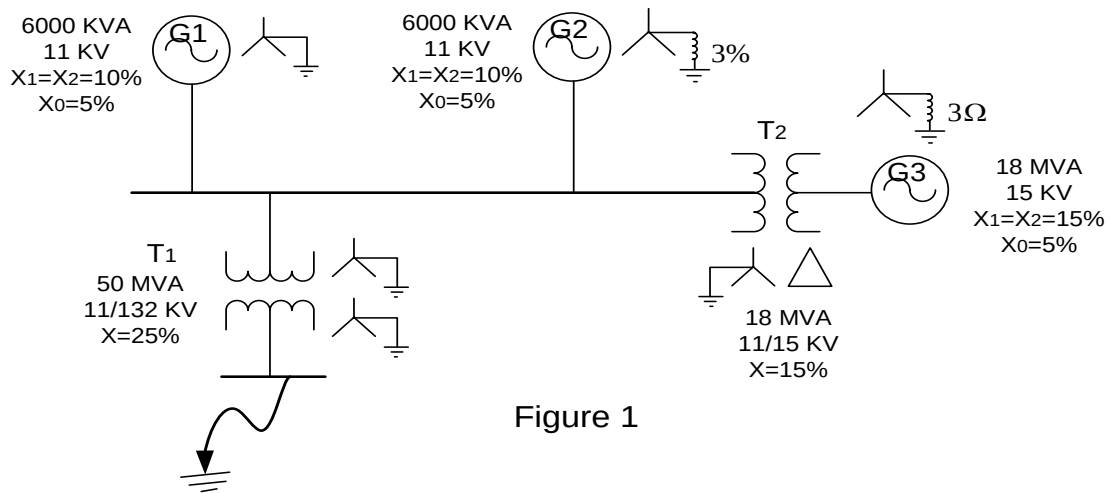


Figure 1

- B** Using appropriate interconnection of sequence networks, derive the equation for a line to line fault in a power system with a fault impedance of  $Z_f$ . [07]
- C** Using appropriate interconnection of sequence networks, derive the equation for a single line to ground fault in a power system with a fault impedance of  $Z_f$ . [07]

\*\*\*