

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Third Semester of B. Tech. Examination (EE)

November 2013

EE207 / EE-207.01 NETWORK ANALYSIS

Date: 21.11.2013, Thursday

Time: 01:30 p.m. To 04:30 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION – I

- Q-1 (a) Name the four different types of dependent sources with their symbols in electric circuits. 01
- (b) (i) Obtain a single current source for the network shown in **figure I**. 01
- (ii) It is known that the potential difference of $12\ \Omega$ resistor in **figure II** is 48 V. Find the entering current I in **Figure II**. 01

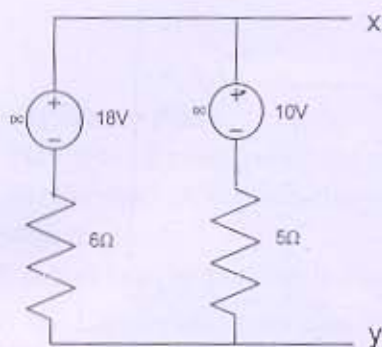


Figure I

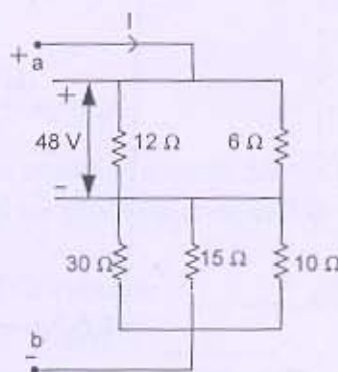


Figure II

- (c) Explain with relevant diagrams: Voltage division and current division rule. 04
- Q-2 (a) Find all the branch currents in the circuit of **figure III** using Nodal Analysis method. 07

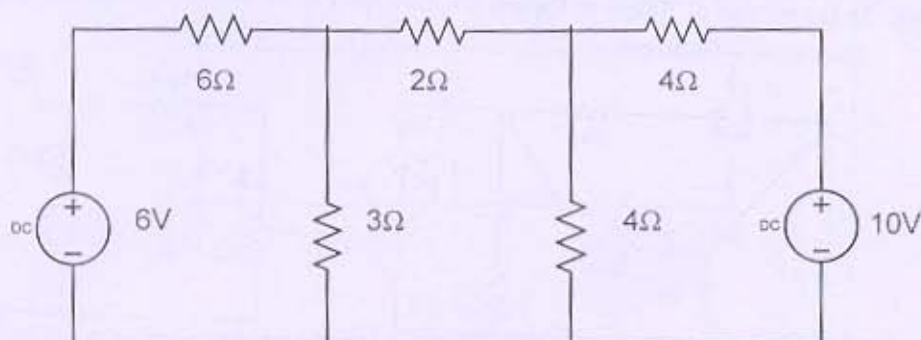


Figure III

- (b) Write relation between Twigs and Links. Also write properties of a Tree in a Graph. 07

OR

Q-2 (a) Determine the current in the 4Ω branch in the circuit shown in the figure IV.

07

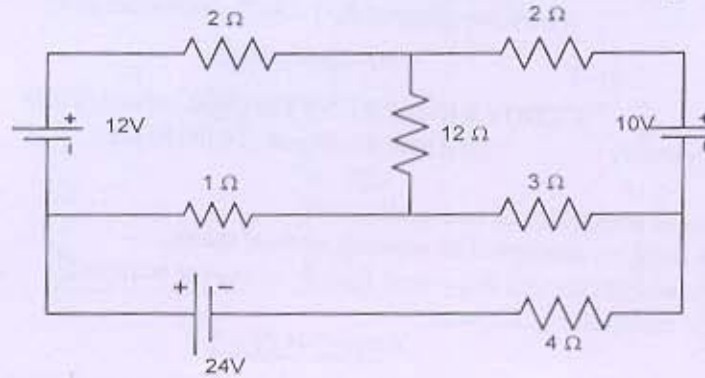


Figure IV

(b) Figure V represents a resistive network. Draw its graph. Select tree and obtain the tie-set matrix.

07

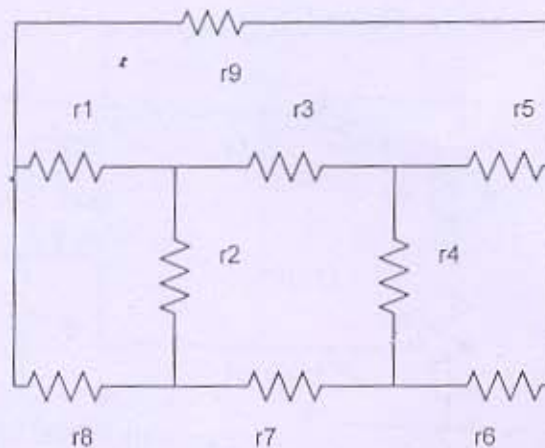


Figure V

Q-3 (a) Write statement of reciprocity theorem. Write the main steps for solving a network utilizing Reciprocity Theorem.

07

(b) In the circuit of figure of figure VI, find the power loss in the 1Ω resistor by Thevenin's Theorem.

07

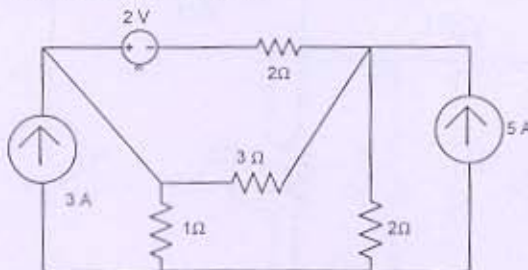


Figure VI

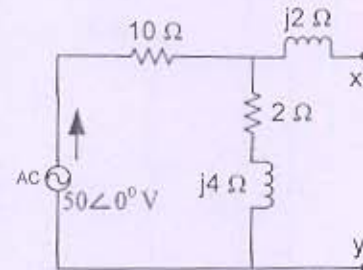


Figure VII

OR

Q-3 (a) Find the Norton's equivalent circuit across x-y terminal. Refer figure VII.

07

- (b) Write statement of Maximum Power Transfer Theorem. Also prove the relevant equation of the Maximum power transfer theorem. 07

SECTION – II

- Q-4(a) Define Gate function with its waveform. Synthesis the following waveform using Gate functions refer **Figure VIII**. 04

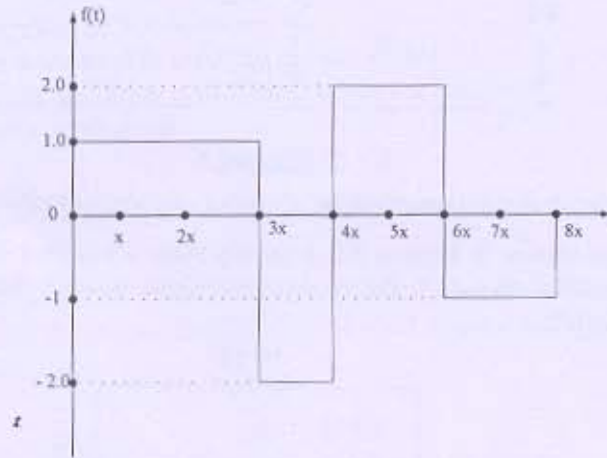


Figure VIII

- (b) State True or False. 01
- (a) For the h parameter being symmetrical the condition must be $\Delta h = -1$.
- (b) For the ABCD parameter being reciprocal the condition must be $AD + BC = 1$. 02
- (c) Fill in the blank.
- i) A unit impulse function is obtained on the differentiation of _____ function.
- ii) The Laplace transformation of $\cos(\omega_0 t + \phi)$ is _____.
- Q-5 (a) Obtain the open circuit parameter from the network shown in **Figure IX** 07

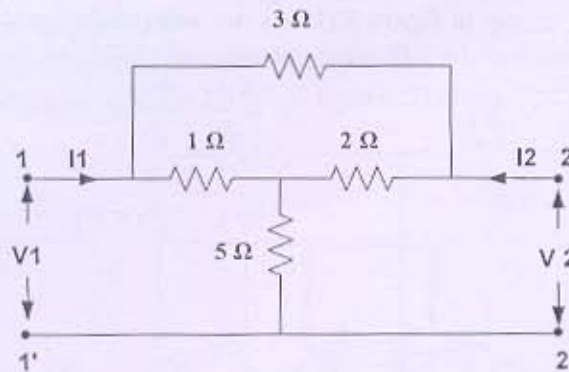


Figure IX

- (b) Derive the relationship between H Parameter and Y parameter. (In both terms.) 07
- OR
- Q-5 (a) A Small signal equivalent circuit of CB mode of BJT is shown in **Figure X**. 07
- Assuming the voltage sources to be independent, find H parameters.

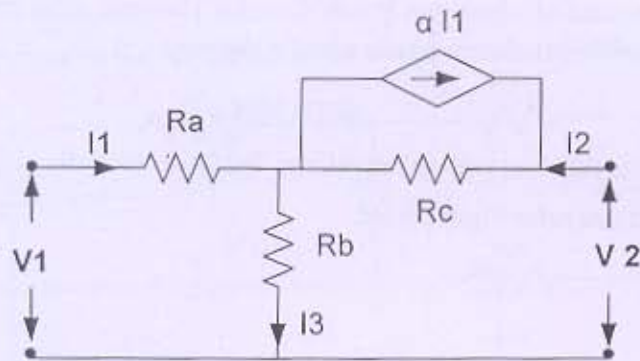


Figure X

- (b) Classify the network configuration by giving its equivalent circuits. 07

Q-6 (a) In the network shown in Figure XI. A steady state is reached with switch K open. At $t=0$, the switch is closed. For the element values given, determine the values of $V_a(0^-)$ and $V_a(0^+)$. 07

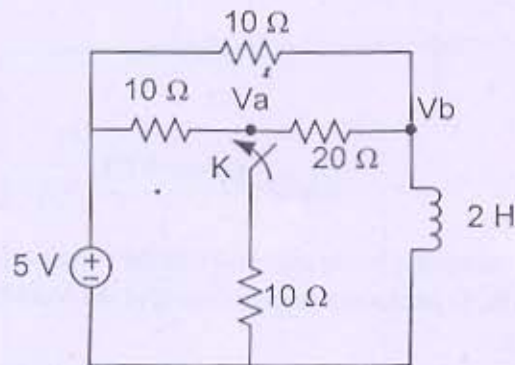


Figure XI

- (b) Derive the equation of current flowing in RC series circuit while giving excitation as a step input. 07

OR

Q-6 (a) The network shown in figure XII has two independent node pairs. If the switch K is opened at $t = 0$, find the following quantities at $t = 0^+$, 07

- (i) V_1, V_2 (ii) $\frac{dv_1}{dt}, \frac{dv_2}{dt}$

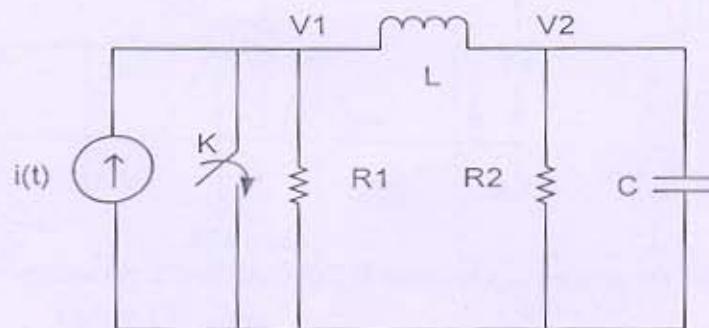


Figure XII

- (b) Prove that $\lim_{s \rightarrow 0} [s F(s)] = \lim_{t \rightarrow \infty} f(t)$. 07