

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Third Semester of Bachelor of Technology (B.Tech.) (E E)

University Examination November 2010

EE207 Network Analysis

Date: 26/11/2010, Friday Time: 10:30 a.m. to 1:30 p.m. Maximum Marks: 70

Instructions:

1. Write both the sections in separate answer books.
2. Take assumptions if required and mention them.

Section – I

		Marks
Q.1	(a) State Thevenin's Theorem. Determine Thevenin's equivalent circuit across terminals AB shown in figure 1 (a).	5
	(b) Determine current flowing through 5Ω resistance in the circuit shown in figure 1 (b) using Norton's Theorem.	5
Q.2	(a) Determine the maximum power delivered to the load in the circuit shown in figure 2.	5
	(b) For the graph shown in fig 3 write the tie-set schedule and obtain the relation between branch currents and link currents.	5
OR		
Q.2	(a) State Norton's theorem. Determine Norton's equivalent circuit for the circuit shown in figure 4.	5
	(b) For the graph given in fig.5 write the cut-set schedule and obtain the relation between tree branch voltages and branch voltages.	5
Q.3	(a) Find z-parameters for the circuit shown in figure 6.	5
	(b) Find ABCD parameters in terms of z parameters for a generalized 2-port network.	5
	(c) Find y parameters in terms of z parameters for a generalized 2-port network.	5
OR		
Q.3	(a) For a general 2-port network find z parameters in terms of y parameters.	5
	(b) Find transmission parameters for a general 2-port network.	5

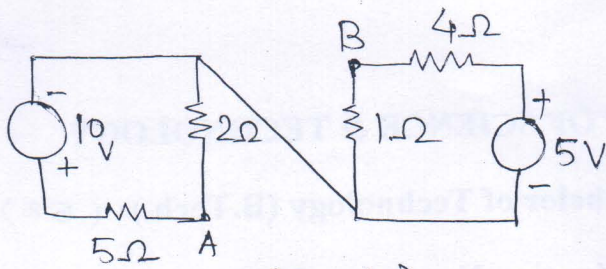


fig 1(a)

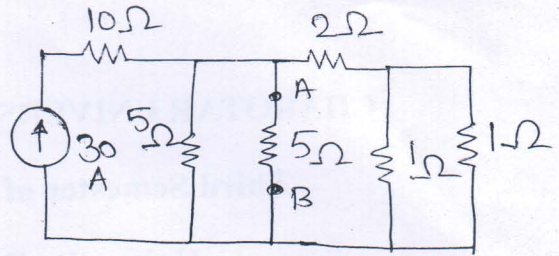


fig 1(b)

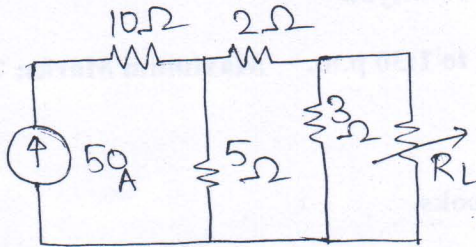


fig 2

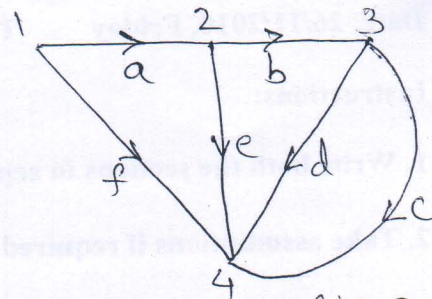


fig 3

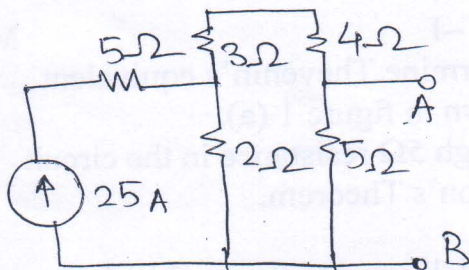


fig 4

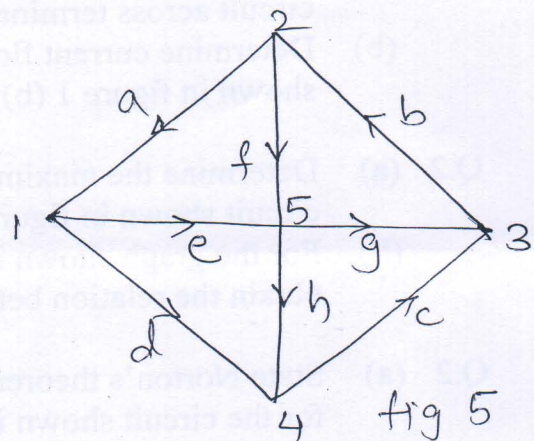


fig 5

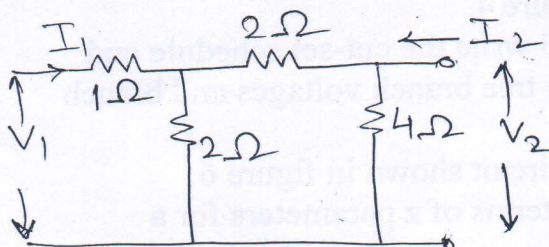


fig 6.

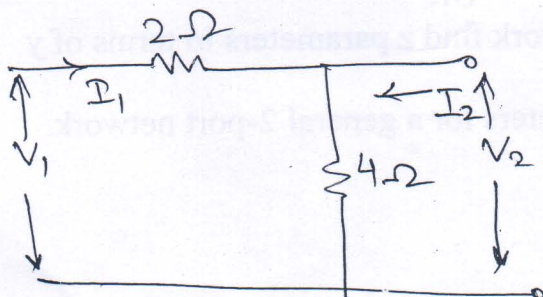


fig 7.

- (c) Find h-parameters for the circuit shown in figure 7. 5

Section-II

- Q.4 (a) Write I_{out} equation in terms of circuit parameters for the figure 8. Find Current gain if $R_2 = R_{in}$. 5

- (b) Define GATE function and write sample expression of it. 5

OR

- Q.4 (a) Find equivalent values of L and C for the circuit shown in figure 9. 5

- (b) Define initial and final value theorem. 5

- Q.5 (a) Find current through 60Ω resistance shown in figure 10 using Nodal Analysis. 7

- (b) Find $V_o(t)$ using Laplace Transform for the circuit of figure 11. 8

OR

- Q.5 (a) Find current through 60Ω resistance shown in figure 10 using Mesh Analysis. 7

- (b) Find loop current expression with no initial conditions for the circuit shown in figure 12 with $V_1 = 5 u(t-1)$ volts. 8

- Q.6 (a) Draw unit impulse, unit step and unit ramp functions delayed by 'T' interval from origin. Write expression of each function. 5

- (b) Write waveform expression for the wave shape shown in figure 13 and find laplace expression of the same. 5

