

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Fourth Semester of B. Tech. Examination (EE)

April 2013

EE203/EE203.01 Electrical Measurement & Measuring Instruments

Date: 25.04.2013, Thursday

Time: 01:30 p.m. To 04:30 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION - I

- Q - 1 (a) Explain in detail different types of phase sequence indicators. [4]
(b) Explain briefly Weston type Synchroscope. [3]
- Q - 2 (a) Draw Equivalent circuit and phasor diagram of Current Transformer. Explain why [7]
C.T. is not operated with secondary side open circuited.
(b) Explain different methods used for localizing ground faults in underground cables. [7]

OR

- Q - 2 (a) Explain briefly difference between C.T. and P.T. State & explain different types of [7]
errors in P.T. and methods to reduce these errors.
(b) A C.T. has a bar primary and 200 secondary winding turns. The secondary winding [7]
burden is an ammeter of resistance 1.2Ω and reactance 0.5Ω , the secondary winding
has a resistance of 0.2Ω and reactance 0.3Ω respectively. The core requires the
equivalent of an mmf of 100 A for magnetization and 50 A for core losses.
(1) Find the primary winding current and ratio error when the ammeter in the
secondary winding circuit indicates 5 A.
(2) How many turns could be reduced in the secondary winding in order that ratio
error be zero for this condition.
- Q - 3 (a) Explain construction of Permanent Magnet Moving Coil type instrument. Also derive [7]
it's general torque equation.
(b) Derive general torque equation for Electrodynamometer type instruments. Also [7]
explain different types of errors in these instruments.

OR

- Q - 3 (a) Explain the operation of Half-wave rectifier type voltmeter. Also explain various [7]
factors affecting the performance of rectifier type instruments.

- (b) Explain with neat diagram operation of attraction type Moving Iron instrument. [7]
Differentiate between PMMC and Moving Iron type instrument.

SECTION – II

- Q - 4 (a) State the difference between accuracy and precision of a measurement. [02]
(b) Explain the observational errors in measurement with suitable example. [02]
(c) Three resistors have the following ratings: [03]

$R_1 = 37 \Omega \pm 5\%$, $R_2 = 75 \Omega \pm 5\%$, $R_3 = 50 \Omega \pm 5\%$. Determine the magnitude and limiting error in ohm and in percent of the resistance if these resistances are connected in series.

- Q - 5 (a) Explain Kelvin's double bridge method for the measurement of low resistance. [5]
(b) A length of cable is tested for insulation resistance by the loss of charge method. An electrostatic voltmeter of infinite resistance is connected between the cable conductor and earth, forming therewith a joint capacitance of 600 pF. It is observed that after charging the voltage falls from 250 V to 92 V in 1 minute. Calculate the insulation resistance of cable. [2]
(c) What are the different difficulties encountered in the measurement of high voltage resistances? Explain how these difficulties are overcome. [3]
(d) The four arms of a Wheatstone bridge are as follows: [4]

$AB = 1000 \Omega$; $BC = 100 \Omega$; $CD = 200 \Omega$ and $DA = 2005 \Omega$

The battery has an emf of 5 V and negligible internal resistance. The galvanometer has a current sensitivity of 10 mm/ μ A and an internal resistance of 100 Ω . Calculate the deflection of galvanometer and the sensitivity of the bridge in terms of deflection per unit change in resistance. Galvanometer is connected across B and D while battery is connected across A and C.

OR

- Q - 5 (a) Derive the general equations for balance of an a.c. bridge. [5]
(b) Explain the working principle of Anderson's bridge and also derive its balance equations. [5]
(c) A Maxwell's Inductance comparison bridge with arm AB consists of a coil with inductance L_1 and r_1 in series with a non-inductive resistance R . Arm BC and coil CD are each a non-inductive resistance of 100 Ω . Arm AD consists of standard variable inductor L and resistance of 32.7 Ω . Balance is obtained when $L_2 = 47.8$ mH and $R = 1.36 \Omega$. Find the resistance and inductance of the coil in arm AB. Detector is connected across B & D while Supply is connected across A & C respectively. [4]

- Q - 6 (a) Explain in detail about the laboratory type DC potentiometer. [7]
- (b) Discuss the applications of AC potentiometer. [7]

OR

- Q - 6 (a) Describe a method for experimental determination of flux density in a specimen of magnetic material using a ballistic galvanometer. Explain how the correction for flux in the air space between the specimen and the coil is applied. [7]
- (b) Explain the method for experimental measurement of magnetizing force acting on a specimen of magnetic material. [7]
