

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Fourth Semester of B. Tech. (EE) Examination

November 2013

EE203/EE203.01 Electrical Measurement & Measuring Instruments

Date: 14.11.2013, Thursday

Time: 01:30 p.m. To 04:30 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION - I

- Q - 1 (a) Explain briefly Nalder Lipman power factor meter. [04]
(b) Write a short note on Electrodynamometer type frequency meter. [03]
- Q - 2 (a) Draw equivalent circuit and phasor diagram of Potential Transformer. Derive actual transformation ratio for potential transformer. [07]
(b) With change in following parameters explain effect on characteristics of Potential Transformer: [07]
- Change in secondary current or VA
 - Change in frequency
 - Change in power factor of secondary burden
 - Change in primary voltage

OR

- Q - 2 (a) Write a short note on mutual inductance method for testing of current transformer. [05]
(b) Write a short note on Varley loop test for localization of cable faults. [05]
(c) A current transformer with a bar primary has 300 turns in its secondary winding. The resistance and reactance of the secondary circuit are 1.5Ω and 1.0Ω respectively including the transformer winding. With 5 A flowing in the secondary winding, the magnetizing mmf is 100 A and the iron loss is 1.2 W. Determine the ratio and phase angle errors. [04]
- Q - 3 (a) Write a short note on repulsion type moving iron instrument. Also, derive general torque equation for moving iron instrument. [07]
(b) Explain construction and operating principle of electro-dynamometer type instrument. [07]
State advantages and disadvantages of electro-dynamometer type instrument.

OR

- Q - 3 (a) Write a short note on quadrant electrometer. State advantages and disadvantages of electrostatic instruments. [06]
(b) State and explain advantages and disadvantages of permanent magnet moving coil type instrument. [04]
(c) Write a short note on megger. [04]

SECTION – II

- Q - 4 (a) Explain relative limiting error. [03]
(b) Explain True value and Precision related to measuring instruments. [04]
- Q - 5 (a) Explain in detail Ammeter-Voltmeter method and Substitution method for measurement of medium order resistance. [07]
(b) What is the procedure of standardisation for slide wire potentiometer? [03]
(c) A basic slide wire potentiometer has a working battery voltage of 3.0 V with negligible internal resistance. The resistance of slide wire is $400\ \Omega$ and its length is 200 cm. A 200 cm scale is placed along the slide wire. The slide wire has 1 mm scale divisions and it is possible to read upto $1/5$ of a division. The instrument is standardized with 1.018 V standard cell with sliding contact at the 101.8 cm mark on scale. Calculate [04]
- Working current
 - The resistance of series rheostat
 - The measurement range
 - Resolution of the instrument

OR

- Q - 5 (a) Explain in detail Gall-Tinsley A.C. potentiometer. Also, mention the errors introduced in measurement by using this potentiometer. [07]
(b) Write short note on following methods for measurement of high resistance: [07]
- Direct deflection method
 - Loss of charge method
- Q - 6 (a) Write a short note on step by step method for determination of B-H curve for ring shaped specimen [05]
(b) Explain operation of Hay's bridge and also derive its balance equations [05]
(c) Explain working of Maxwell's inductance bridge. [04]

OR

- Q - 6 (a) Explain in detail magnetic potentiometer. [05]
(b) Explain working of Schering bridge and also derive its balance equations. [05]
(c) The arms of a five node bridge are as follows: [04]
Arm ab consists of unknown impedance (R_1, L_1) in series with a non-inductive variable resistor r_1 . Arm bc consists of resistor $R_3 = 100\ \Omega$. Arm cd consists of $R_4 = 200\ \Omega$. Arm da consists of $R_2 = 250\ \Omega$. Arm de consists of a variable resistor r . Arm ec consists of loss-less capacitor $C = 1\ \mu\text{F}$, and arm be consists of a detector. An a.c. supply is connected between a and c. Calculate R_1 and L_1 when under balance conditions $r_1 = 43.1\ \Omega$ and $r = 229.7\ \Omega$
