

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Fourth Semester of Bachelor of Technology (B.Tech.)

University Examination May 2011

EE 206 Digital Electronics and Microprocessors

Date: 13/05/2011, Friday

Time: 10:00 a.m. to 1:00 p.m.

Maximum Marks: 70

Instructions:

1. Write both the sections in separate answer sheets.
2. Clearly mention the assumptions if any.

SECTION-I

Marks


- Q.1 (a) Write the Boolean algebraic laws. 2
(b) Do as directed. 6
 I) Multiply 1101_2 by 110_2
 II) Convert 4057.06_8 to decimal.
 III) Convert 1011011011_2 to hexadecimal.
(c) I) Each term in the standard SOP form is called a _____. 2
 (a) minterm (b) maxterm (c) Don't care (d) literal
 II) The code used for labeling the cells of a k-map is _____.
 (a) 8-4-2-1 binary (b) hexadecimal (c) gray (d) octal
- Q.2 (a) What are the merits and demerits of C-MOS? 4
(b) Reduce using mapping the expression $f = \sum m(0, 1, 3, 4, 5, 6, 7, 13, 15)$ and implement the real minimal expression in universal logic. 6
- OR
- Q.2 (a) With the help of a neat diagram explain the working of a 2-input TTL NAND Gate. 4
(b) Simplify the following expression once by considering the don't care condition and once by ignoring the don't care condition. 6
 $Y = \sum m(1, 4, 8, 12, 13, 15) + d(3, 14)$.
- Q.3 (a) Explain a BCD to 7-segment decoder using 4-line to 16-line decoder with diagram and truth table. 4
(b) Build a full adder from half adder circuit and also draw its truth table. 4
(c) With a neat diagram explain the operation of a 4-bit SISO register. Draw the timing diagram and give its truth table. 4
(d) What is counter? What are its types? What are the applications of a counter? 3
- OR
- Q.3 (a) Implement the following Boolean expression using 8:1 multiplexer. 4
 $f(A, B, C, D) = A'B'D' + ABC + B'CD + A'CD$
(b) Explain with diagram the working of D-type flip flop. Give its truth table. 4
(c) Explain working of 2-bit asynchronous binary up counter using T-Flip flop with suitable circuit and timing diagram. 4
(d) Explain 3 to 8-line decoder. 3

SECTION-II

- Q.4 (a) Explain the following terms in brief. 5
1. Microprocessor
 2. Compiler
 3. Address bus
 4. Data bus
 5. Flag Register

- (b) Explain the execution of CALL instruction in 8085 microprocessor. 6

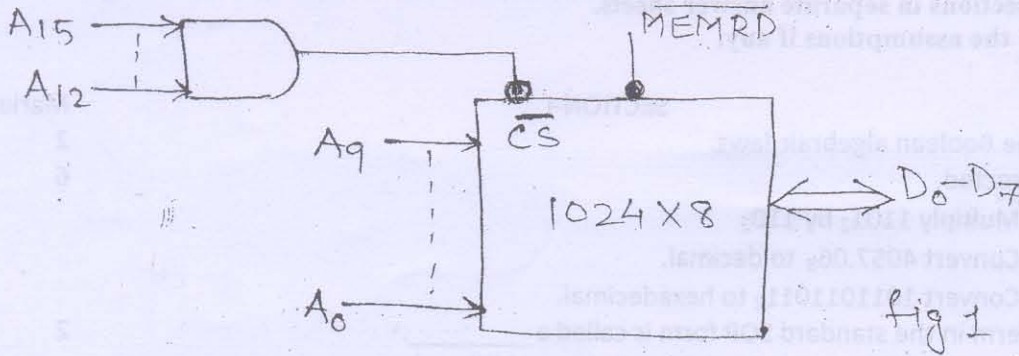
- Q.5 (a) Explain partial address decoding. Find memory map of the memory chip shown in fig. 1 6



- (b) Draw the timing diagram for LDA 2500h instruction. 6

OR

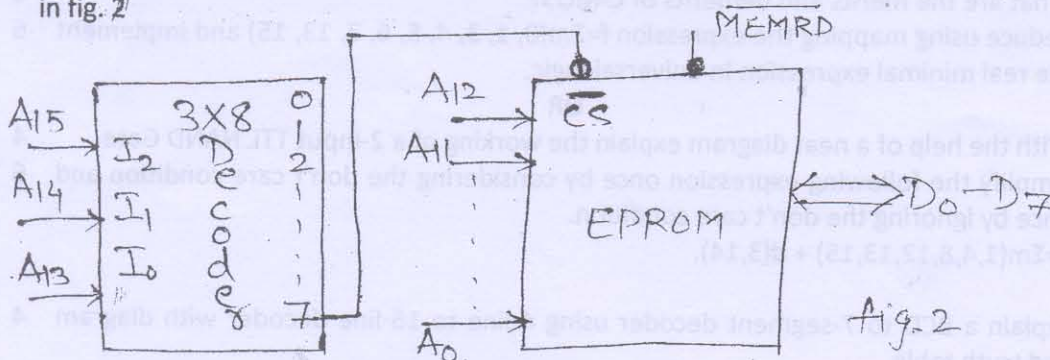- Q.5 (a) Explain absolute address decoding. Find memory map of the memory chip shown in fig. 2 6



Line 7 is low when $A_{15} \rightarrow A_{13}$ are high.

- (b) Draw the timing diagram for STA 2400h instruction. 6

- Q.6 Write 8085 microprocessor based assembly program for any three of the following. 12

Explain the program logic in brief.

- (a) To sort the given array of data in descending order.
- (b) Find the total number of bytes having MSB and LSB as 1 from the given array of data 8-bit data.
- (c) Delay subroutine to have delay of 10 ms with external clock frequency of 3 MHz.
- (d) Discard all the negative numbers and add rest of the data bytes from the given array of 8-bit data. Store the result (sum and carry) in two consecutive memory locations.
- (e) Copy the block of data starting from 2300 H to the memory location 2400 H.
- (f) Discard all odd numbers from the array of 8-bit data and add rest of the numbers.