

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Fifth Semester of B. Tech. Examination (EE)

November 2012

EE 305 Power Electronics & Drives - I

Date: 30.11.2012, Friday

Time: 10:00 a.m. To 01:00 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION - I

- Q - 1 (a) Explain V-I Characteristics of G.T.O. Also explain disadvantages of G.T.O. [05]
(b) State different types of Power Electronic Converters. [02]
- Q - 2 (a) Explain briefly Switching Characteristics of Thyristor. [04]
(b) Explain with a neat diagram Static V-I Characteristics of a Thyristor. [04]
(c) State and Explain briefly different types of ratings for Thyristor. [06]

OR

- Q - 2 (a) Write a Short note on protection of Thyristor. [04]
(b) What is String efficiency? Explain briefly parallel operation of SCRs. [06]
(c) It is required to operate 250 A SCR in parallel with 350 A SCR with their respective on-state voltage drops of 1.6 V and 1.2 V. Calculate the value of resistance to be inserted in series with each SCR so that they share the total load of 600 A in proportion to their current ratings. [04]
- Q - 3 (a) Explain with neat waveforms operation of UJT based Ramp triggering circuit. Also explain the effect of variation in charging resistor on output pulses. [06]
(b) Explain in detail driver circuit for BJT [04]
(c) Explain in detail Complementary Commutation technique for Thyristor. [04]

OR

- Q - 3 (a) What is the difference between triggering and commutation of Thyristor? Explain briefly External Pulse Commutation technique used for Thyristor. [04]
(b) Explain with neat waveforms resistance firing of an SCR. [04]
(c) List out the requirements of a BJT driver circuit. Explain driver circuit for MOSFET. [06]

SECTION - II

- Q - 4 (a) Explain with output voltage and current waveforms operation of step down chopper. [04]
(b) A step-up chopper has input voltage of 220 V and output voltage of 660 V. If the non-conducting time of thyristor-chopper is 100 μ s, compute the pulse width of output [03]

voltage. In case pulse width is halved for constant frequency operation, find the new output voltage.

- Q - 5 (a) Explain operation of Two-quadrant type-A and Two-quadrant type-B Chopper [07]
(b) Explain in detail with neat waveforms operation of 1- Φ , Full wave, Full converter controlled DC series motor. [07]

OR

- Q - 5 (a) Explain in detail with neat waveforms chopper control of separately excited DC Motor. [07]
(b) Explain with neat waveforms operation of Current-Commutated Chopper. [07]
Q - 6 (a) Explain in detail with neat waveforms of Supply Voltage, Load Voltage, Load Current and Thyristor Current, operation of 3- Φ , Full Wave, Fully Controlled Bridge Rectifier with R-L load for firing angle $\alpha = 30^\circ$ & 90° . [07]
(b) A 1- Φ , 230 V, 1 KW heater is connected across 1- Φ , 230 V, 50 Hz supply through an SCR. For firing angle delays of 45° and 90° , calculate the power absorbed in the heater element. [03]
(c) Write Short note on Extinction angle control scheme for power factor improvement of Phase controlled rectifiers. [04]

OR

- Q - 6 (a) Explain with neat waveforms the operation of 1- Φ , Semiconverter with R-L load for continuous load current. Also derive equation of Average and RMS value of output voltage. [07]
(b) Explain in detail operation of Dual Converter with and without circulating current. [07]
