

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Sixth Semester of B. Tech. Examination (EE)

Nov/Dec 2012

EE310 Programmable Logic Controller and Industrial Automation

Date: 09.11.2012, Friday

Time: 10:00 a.m. To 01:00 p.m.

Maximum Marks: 70

Instructions:


1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION - I

- Q - 1 (a) Draw and explain block diagram of PLC in detail [06]
(b) List the types of counters available in PLC [01]
- Q - 2 (a) Draw and explain working of ON delay timer (along with timing diagram). Write a program in PLC for flashing of a light for 1sec. (Light will go on for 1sec after that will turn off for 1 sec, and the process will go on.) [12]
(b) State function of input module. [02]

OR

- Q - 2 (a) Draw and explain working of OFF delay timer (along with timing diagram). [06]
(b) Three conveyors feed a main conveyor. The count from each feeder conveyor is fed into an input register in PLC. Construct a PLC program to obtain the total count of parts on the main conveyor. [06]
(c) State function of output module. [02]
- Q - 3 (a) With the help of necessary figure explain in detail scan cycle of PLC [06]
(b) Make ladder diagram for the following sequence: [06]
When SW1 is closed, CR1 goes on
After CR1 goes on, SW2 can turn CR2 on
When CR2 goes on, PL1 goes off
(c) State the name of following symbols: [02]

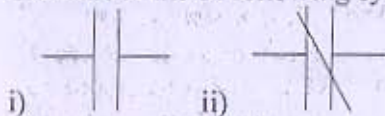

OR

- Q - 3 (a) Implement logic gates in PLC in ladder logic. (AND, OR, NOT, NOR, NAND, EXOR and EXNOR) [14]

SECTION - II

- Q - 4 (a) Do as directed: [07]
i. Define transducer

- ii. Define sensor
- iii. State the range of standard current signal used for transmission in PLC
- iv. Battery in the PLC is used for ____.
- v. What is the difference between, sink and source module?
- vi. What sort of voltages are generally used for PLC input's and output's?
- vii. What is the basic difference between a PLC and relay control system?


- Q - 5 (a)** State the advantages and disadvantages of PLC system [10]
(b) When a switch is turned on, C goes on immediately and D goes on 9 seconds later. [04]
 Opening the switch turns both C and D off.

OR


- Q - 5 (a)** For the following questions below convert the word description to gate symbols and [09]
PLC ladder logic diagram:
- i. Switch 8 and switch 11, plus either switch 22 or switch 34, must be on for output 67 to be on.
 - ii. For output 7 to be on, input 6 must be off and either input 8 or input 9 must be on. In addition, one of inputs 1, 2 or 3 must be on.
 - iii. For output H to be on and both inputs C and D must be off. In addition one or more inputs E, F and G must be off.
- (b)** List the types of programming languages used to program a PLC. Write two lines [05]
 about each one of them.

- Q - 6 (a)** Do as directed: [06]

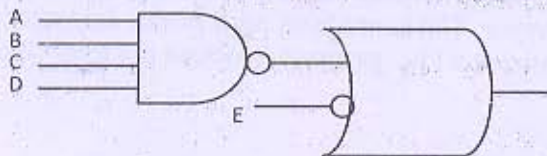
- i. Prepare ladder logic for the following:



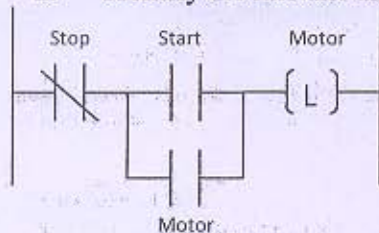- ii. Identify the mistake and rectify it.



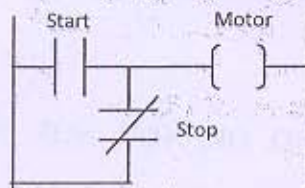- iii. Prepare gate symbol for the following if possible



- iv. With the increase in the length of wire current ____.
- v. What is the full form of HMI
- vi. Which of the following is not normally in the array of status indicators found on the processor module:
 a) Memory OK

- b) Wiring OK
- c) Battery OK
- (b) There are two conveyors, each with sensors to count input and output of parts entering and leaving the conveyors. Prepare a ladder logic to glow three indicating lights for the process as follows: [06]
 - Number of parts on the both the conveyors equal - White light
 - Number of parts on conveyor 1 greater than conveyor 2 - Green light
 - Number of parts on conveyor 2 greater than conveyor 1 - Blue light
- (c) Prepare a ladder diagram for an output is on if the input count is less than 34 or more than 41. [2]

OR

Q - 6 (a) Multiple Choice questions:

[05]

1. What do the letters 'AQ' normally stand for in PLC addresses?
 - a) Anything Quaint
 - b) Analog out of Range
 - c) Analog Output
 - d) Nothing, it is no typical or common use in PLC's
2. What does 'X' normally stand for in PLC addresses?
 - a) Timer
 - b) Counter
 - c) Digital Output
 - d) Digital Input
3. What does 'Q' normally stand for in PLC addresses?
 - a) Timer
 - b) Digital Input
 - c) Counter
 - d) Digital Output
4. What time delay do a timer preset of 33 & a time base of 0.01 give you?
 - a) 33 seconds
 - b) 0.33 seconds
 - c) 3.3 seconds
 - d) Nothing, this question doesn't make any sense
5. PLC's does a self-check every scan cycle.
 - a) True
 - b) False
- (b) A machine M is to be turned on either when a count A goes up to 11 or when count B goes up to 16. One stop button or switch resets the entire process. [05]
- (c) A fan is to be started and stopped from any one of the three locations. Each location has a start and a stop button. Prepare ladder logic for the same. [04]
