

CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Sixth Semester of B. Tech. Examination (EE)

May 2012

EE 310 Programmable Logic Controller & Industrial Automation

Date: 11.05.2012, Friday

Time: 01:30 p.m. To 04:30 p.m.

Maximum Marks: 70

Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

SECTION - I

Q - 1 State and Explain Advantages and Disadvantages of PLC. [07]

Q - 2 (a) Explain major units of a PLC. Also draw PLC system layout. [07]

(b) Explain DC Input Module and AC Input module. [07]

OR

Q - 2 (a) Explain PID module with its block diagram. [05]

(b) Explain 8 bit ADC converter with Digital Step diagram. [04]

(c) Draw and Explain PLC CPU power supply. [05]

Q - 3 (a) Using Ladder diagram make NOT, OR, AND, NAND, NOR, EX-OR and EX-NOR Gate. [09]

(b) What are the different types of Input and Output circuits? Explain each. [05]

OR

Q - 3 (a) Describe TON, TP and TOFF blocks available in Codesys V2.3 [06]

(b) State the D-Morgan's theorem. And prove it by making ladder logic in PLC. [08]

SECTION - II

Q - 4 Draw and explain PLC Process scanning in detail. [07]

Q - 5 (a) Write down the program for the following logic: [10]


A wood saw W, a fan F and a Lube pump P, all go on when a start button is pushed. A stop button stops the saw only. The fan is to run an additional 5 seconds to blow the chips away. The lube pump is to run for 8 seconds after shutdown of W. Additionally, if the saw has run more than one minute, the fan should stay on indefinitely. The fan may then be turned off by pushing a separate fan reset button. If the saw has run less than one minute, the pump should go off when the saw is turned off. The 8 second time delay off does not take place for a running time of less than 1 minute.

(b) Write down the program for the following logic: [04]

There are three mixing devices on a processing line: A, B and C. After process begins, mixer A is to start after 7 seconds elapse. Next, mixer B is to start 3.6 seconds after mixer A. Mixer C is to start 5 seconds after B. All then remain on until a master enable switch is turned off.

OR

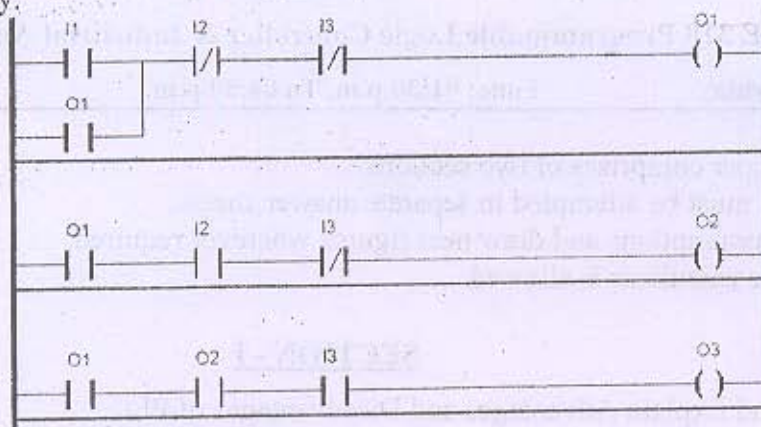- Q - 5 (a) For the Given ladder logic diagram write down the output (O1, O2 and O3) is TRUE [06]
or FALSE for the given input (I1, I2 or I3) condition. All Logic should be done in
sequence only.



Seq. No.	Input Conditions			Output coils		
				O1	O2	O3
1	I1: TRUE	I2: FALSE	I3: FALSE			
2	I1: FALSE	I2: FALSE	I3: FALSE			
3	I1: FALSE	I2: TRUE	I3: FALSE			
4	I1: FALSE	I2: TRUE	I3: TRUE			

- (b) A Thermo-couple is connected to a 16 bit Analog Input module. Maximum input [08]
voltage of Analog input module is 24 V DC. Assume that for 0° C to 200° C thermo-
couple gives 0 V to 20 V DC linearly. At output digital module 5 nos. of Fans are
connected. So write down the program for the following given logic.
When temperature is (i) $\geq 0^{\circ}\text{C}$ but $< 40^{\circ}\text{C}$, One fan is on. (ii) $\geq 40^{\circ}\text{C}$ but $< 80^{\circ}\text{C}$,
two fans are on (iii) $\geq 80^{\circ}\text{C}$ but $< 120^{\circ}\text{C}$, three fans are on (iv) $\geq 120^{\circ}\text{C}$ but $< 160^{\circ}\text{C}$,
four fans are on (v) $\geq 160^{\circ}\text{C}$ all fans are on.

- Q - 6 (a) Write Down a program using Timer block (TON, TOF or TP) for the following bulb [08]
series as shown in Figure 1.

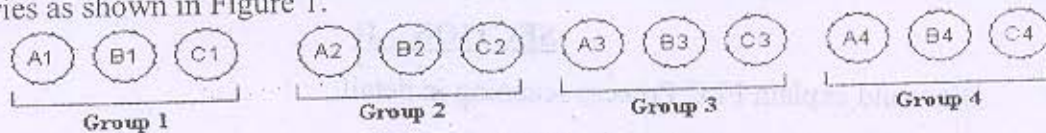


Figure 1

Group 1 on for 150ms (at that time all other groups are off), after that group 2 is on
for next 150ms (at that time all other groups are off), after that group 3 is on for next
150ms (at that time all other groups are off), after that group 4 is on for next 150ms
(at that time all other groups are off). After this all process is repeated until processor
is on.

- (b) What are the factors to be considered in selecting a PLC? Describe each in short. [06]

OR

- Q - 6 (a) Explain CTU, CTD and CTUD function block. Draw the timing diagram of CTU. [08]

- (b) Explain Memory map organization with necessary diagram. [06]
