

# CHAROTAR UNIVERSITY OF SCIENCE & TECHNOLOGY

Second Semester of M. Tech. Examination (EE)

May 2013

EE 708 Advanced Power Electronics in Power System

Date: 15/05/2013, Wednesday

Time: 10:00 a.m. To 01:00 p.m.

Maximum Marks: 70

## Instructions:

1. The question paper comprises of two sections.
2. Section I and II must be attempted in separate answer sheets.
3. Make suitable assumptions and draw neat figures wherever required.
4. Use of scientific calculator is allowed.

## SECTION - I

- Q - 1 (a) Explain briefly working of shunt active power filter. And also compare it with series active power filter. [04]
- (b) Enlist and discuss the various performance parameters of line commutated converters. [03]
- Q - 2 (a) A 3- $\Phi$  bridge inverter delivers power to a resistive load from a 450 V dc source. For a star connected load of  $10\ \Omega$  per phase, determine for both (a)  $180^\circ$  mode and (b)  $120^\circ$  mode : [07]
- RMS value of load current
  - RMS value of thyristor current
  - Load power
- (b) Explain working of 24 -pulse converter. [07]

## OR

- Q - 2 (a) Explain in detail operation of 3- $\Phi$ , 3-level Diode-clamped inverter supplying star connected resistive load. Also explain the role of clamping diodes. [07]
- (b) Explain in detail advantages of multi-level inverters over conventional two-level inverters. Explain operation of one leg of 3-level Cascaded H-bridge Inverter. [07]
- Q - 3 (a) Explain with neat current and voltage waveforms rectifier operation of 3- $\Phi$ , Full wave diode based current source converter. [07]
- (b) Explain with a neat block diagram synchronous reference frame theory for generation of reference compensating currents. [07]

## OR

- Q - 3 (a) Explain in detail operation of 3- $\Phi$ , Bridge type current source inverter feeding an induction motor. [07]
- (b) Derive the equation for reference compensating currents using instantaneous reactive power theory and also discuss in brief hysteresis current control technique. [07]

## SECTION - II

- Q - 4 (a) Explain briefly series compensation. [03]
- (b) Explain briefly working of Unified Power Flow Controller. [04]
- Q - 5 (a) Explain in detail the objective of shunt compensation when connected at the [07]

mid-point and at the end of a transmission line.

- (b) Explain working of thyristor controlled reactor. Also explain different solutions for reducing the harmonics generated by thyristor controlled reactor. [07]

OR

- Q - 5 (a) Explain with neat waveforms working of thyristor switched capacitor. Also explain conditions for transient free switching of thyristor switched capacitor. [07]

- (b) Draw operating V-I area for Fixed Capacitor-Thyristor Controlled Reactor (FC-TCR) and Thyristor Switched Capacitor-Thyristor Controlled Reactor (TSC-TCR). Also explain functional control scheme for FC-TCR and TSC-TCR. [07]

- Q - 6 (a) Explain in detail operation of GTO Thyristor Controlled Series Capacitor (GCSC). [07]

- (b) Explain in detail Overall control structure of Unified Power Flow Controller. [07]

OR

- Q - 6 (a) Explain with neat diagram working of static synchronous series compensator. [07]

- (b) Draw and explain control scheme for two converter based Interline Power Flow Controller. [07]

\*\*\*\*\*